
22-R-VIB-JL-47

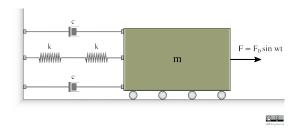A mass of m=27 kg is supported by rollers and has a periodic force of $F=4\sin 5t$ N applied to it. Two springs in series, each with stiffness k=42 N/m and two dampers in parallel, each with a damping constant c=9 N·s/m attached to the wall keep the block in steady-state vibration.



Find the equivalent values for mass \mathbf{m} , stiffness \mathbf{k} , and damping \mathbf{c} if there was only one of each component in the circuit, and select their proportionality to inductance \mathbf{L} , resistance \mathbf{R} , and capacitance \mathbf{C} respectively.

Select the circuit diagram that represents the damped forced system's electrical equivalent.

Solution

Calculating the mass, spring stiffness and damping equivalent we have:

$$m_{eq} = m = 27 \text{ [kg]}$$

$$k_{eq} = \left(\frac{1}{k} + \frac{1}{k}\right)^{-1} = \frac{k}{2} = 21 \text{ [N/m]}$$

$$c_{eq} = c + c = 2c = 18 \text{ [N·s/m]}$$


Then inductance L, resistance R, and capacitance C of the equivalent electrical analog system is given by:

L = m in units of [H]

 $C = \frac{1}{k_{eq}}$ in units of [F]

 $R = c_{eq}$ in units of $[\Omega]$

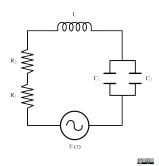Lastly creating the equivalent circuit, the equivalent inductance is a single inductor with inductance L=m. The equivalent resistance is 2 resistors in series each with resistance R=c for an equivalent resistance of $R_{eq}=2R=2c$. And the equivalent capacitance is 2 capacitors in parallel each with capacitance $C=\frac{1}{k}$ for an equivalent capacitance $C_{eq}=2C=\frac{2}{k}$ (shown below).



Device	Equivalent Series Connection	Equivalent Parallel Connection
Resistors	$R_{\rm eq} = R_{\rm l} + R_{\rm 2} + \cdots + R_{\rm N}$	$\frac{1}{R_{sq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$
Capacitors	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$	$C_{eq} = C_1 + C_2 + \dots + C_t$
Inductors	$L_{eq} = L_1 + L_2 + \cdots + L_N$	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}$